

Exercise Five - P2

23. Draw the logic diagram of 2-to-4 line decoder using :-

- (1) NOR gates . active high decoder
- (2) NAND gates . active low decoder


A	B	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$D_0 = A'B' = [(A'B)']' = (A+B)'$$

$$D_1 = A'B = [(A'B)']' = (A+B')'$$

$$D_2 = AB' = [(AB')']' = (A'+B)'$$

$$D_3 = AB = [(AB)']' = (A'+B')'$$

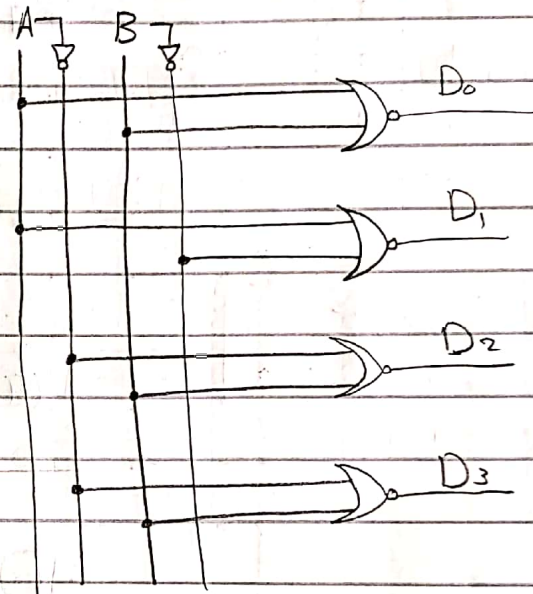


A	B	D_0	D_1	D_2	D_3
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

$$D_0 = A+B = [(A+B)']' = (A'B)'$$


$$D_1 = A+B' = [(A+B')']' = (A'B)'$$

$$D_2 = A'+B = [(A'+B)']' = (AB')'$$


$$D_3 = A'+B' = [(A'+B')']' = (AB)'$$

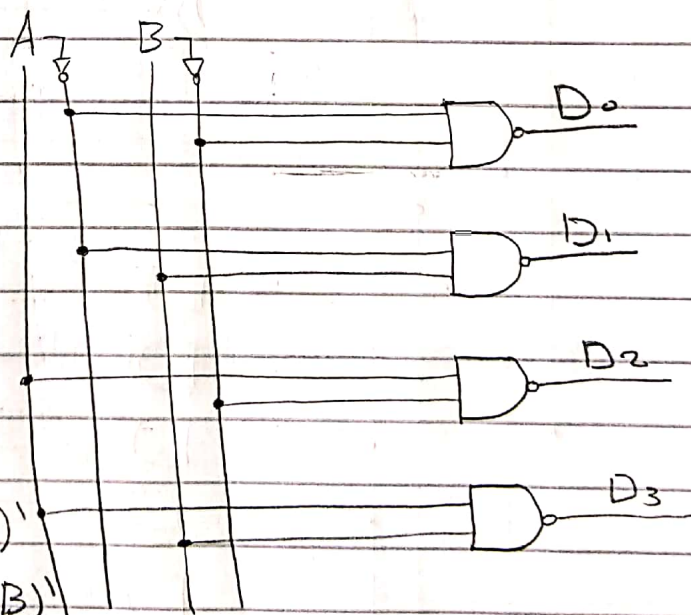


24- Design a BCD-to-Decimal decoder using the unused combinations of the BCD code as don't-care conditions:-

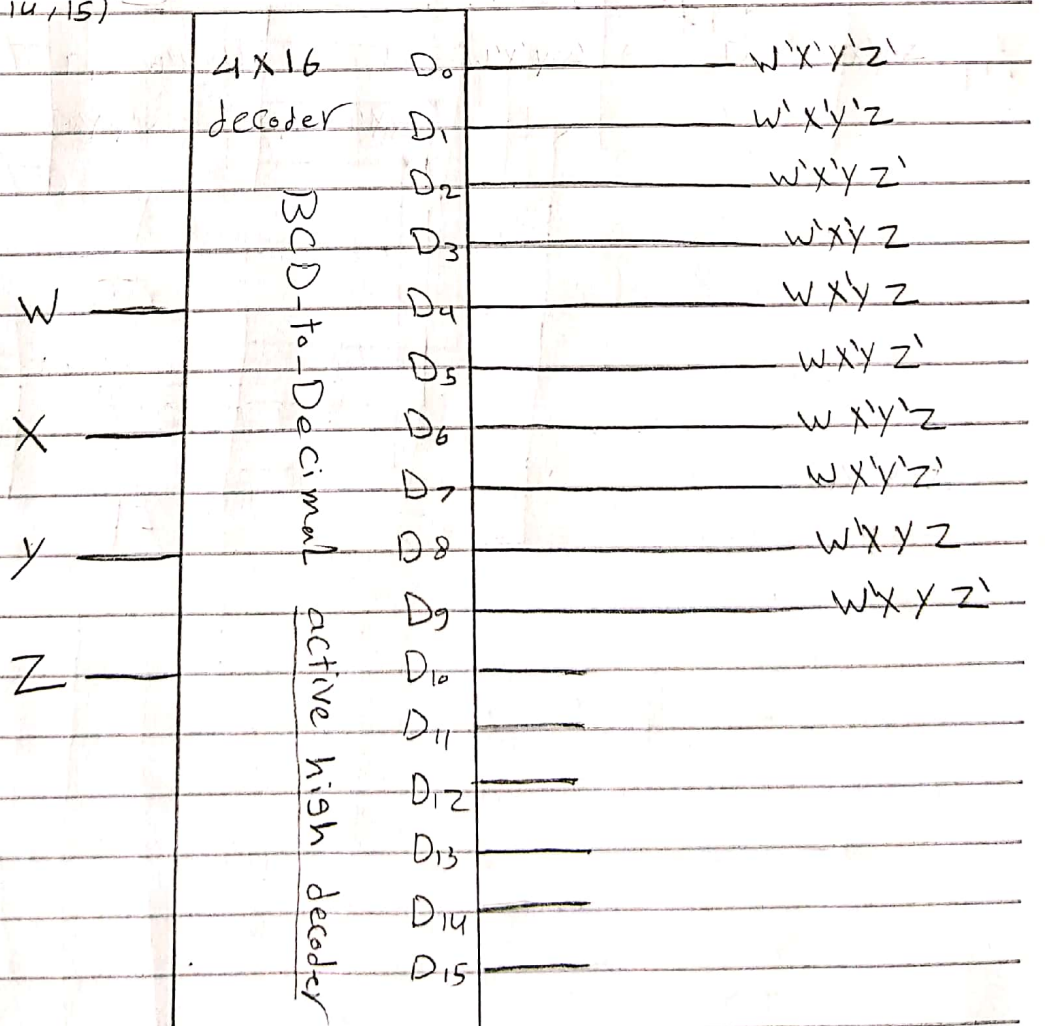[illegible]
$$d = \sum (10, 11, 12, 13, 14, 15)$$

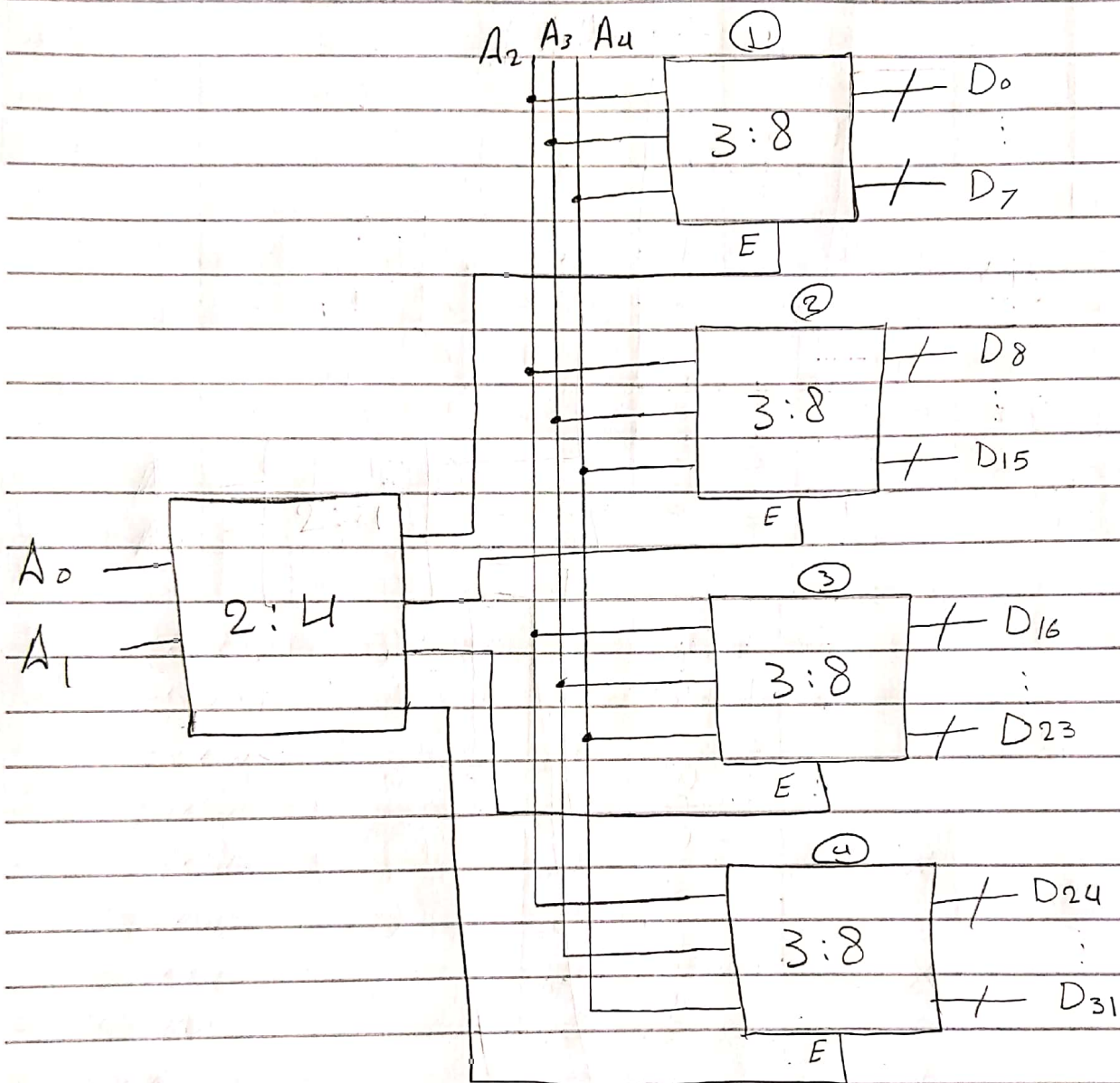
25- Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder. Use block diagrams for the components:



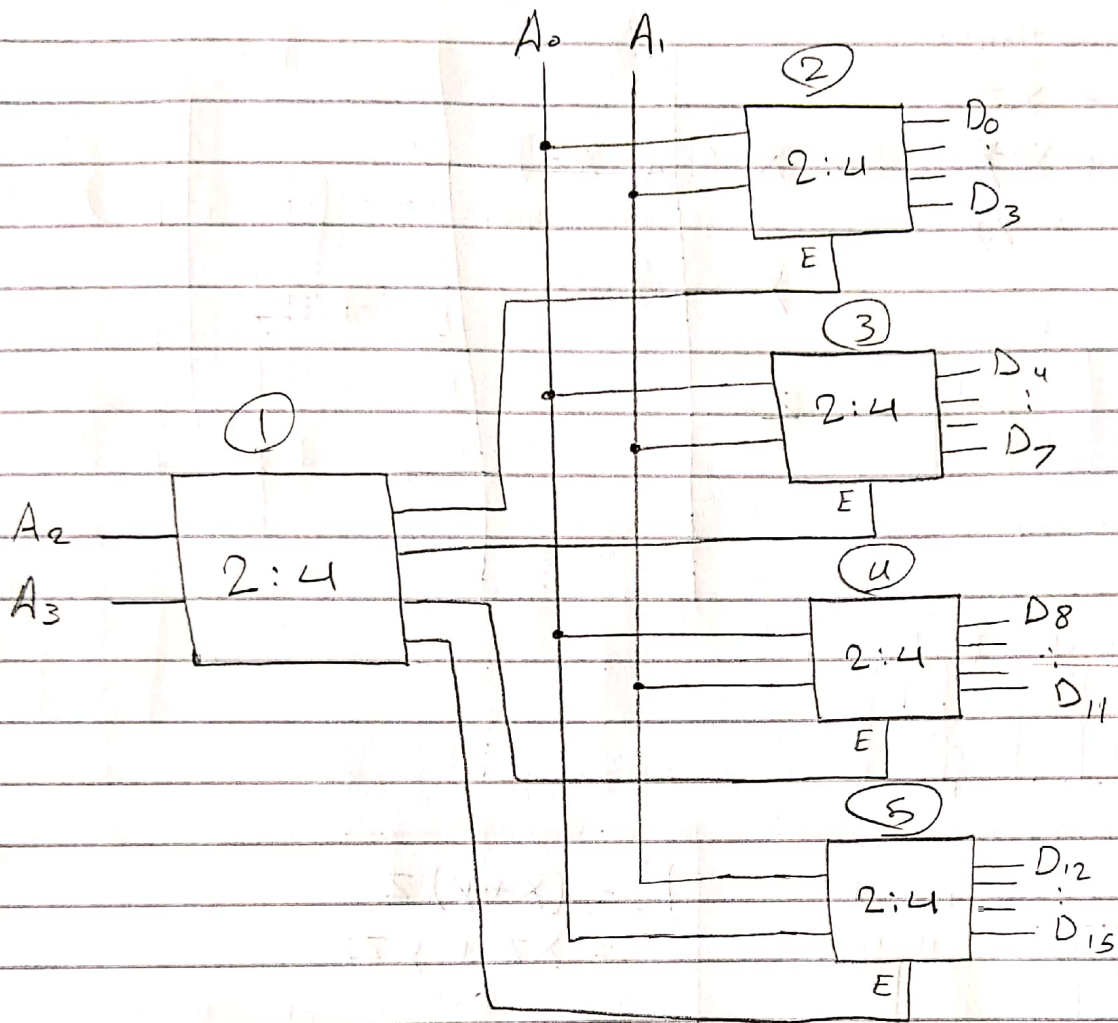26. Construct a 4-to-16-line decoder with five 2-to-4 line decoders with enable.




27. A Combinational Circuit is specified by the following three Boolean Functions:

$$F_1 = \sum (1, 4, 6)$$

$$F_2 = \sum (3, 5)$$

$$F_3 = \sum (2, 4, 6, 7)$$

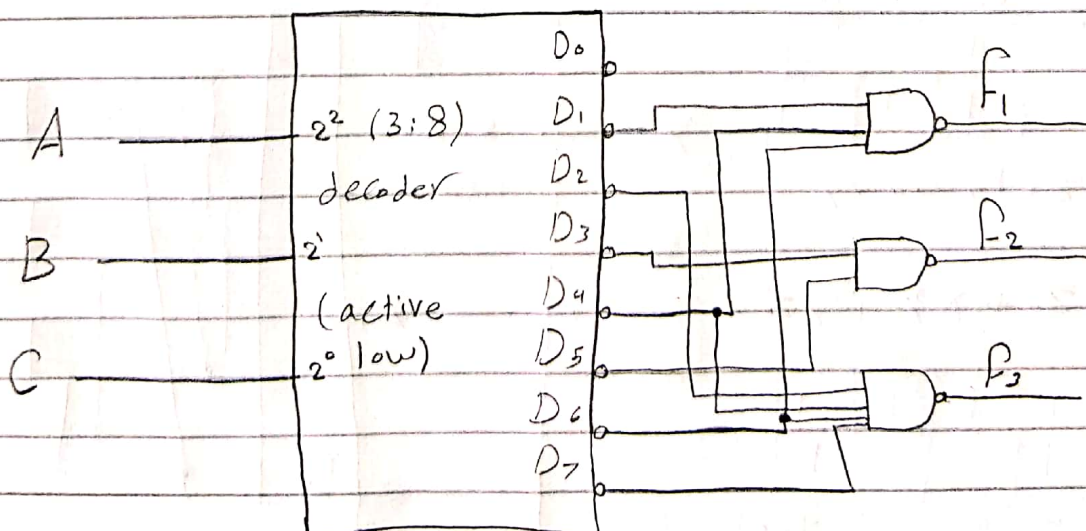Implement the circuit with a decoder constructed with NAND gates.



28- Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions:


(a) $F_1 = X'Y'Z' + XZ$

$F_2 = XY'Z' + X'Y$

$F_3 = X'Y'Z' + XY$

X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_1 = \Sigma(2, 5, 7)$

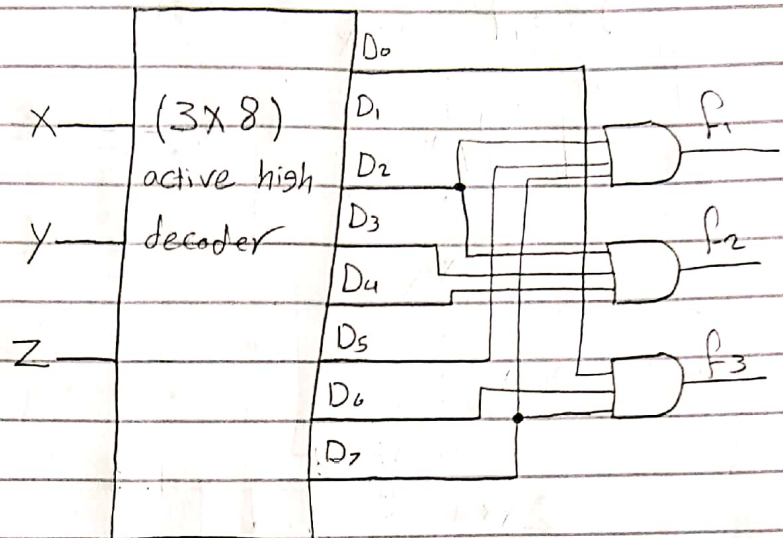

X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_2 = \Sigma(2, 3, 4)$

X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_3 = \Sigma(0, 6, 7)$

$F_3 = (X+Y)Z$
 $= XZ + YZ$

X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_3 = \Sigma(3, 5, 7)$

(b) $F_1 = (Y' + X)Z$

$= Y'Z + XZ$


X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_1 = \Sigma(1, 5, 7)$


$F_2 = Y'Z' + X'Y + YZ'$

X \ YZ	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$F_2 = \Sigma(0, 1, 2, 3, 4, 6)$

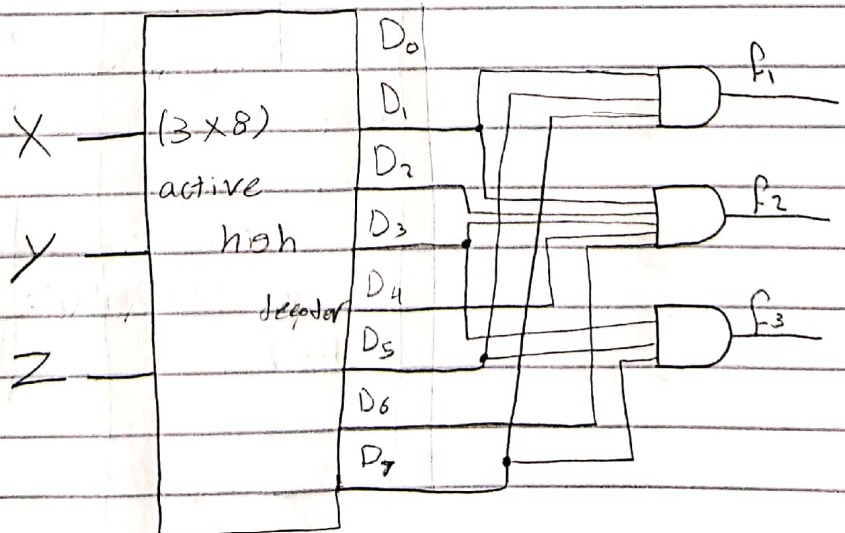

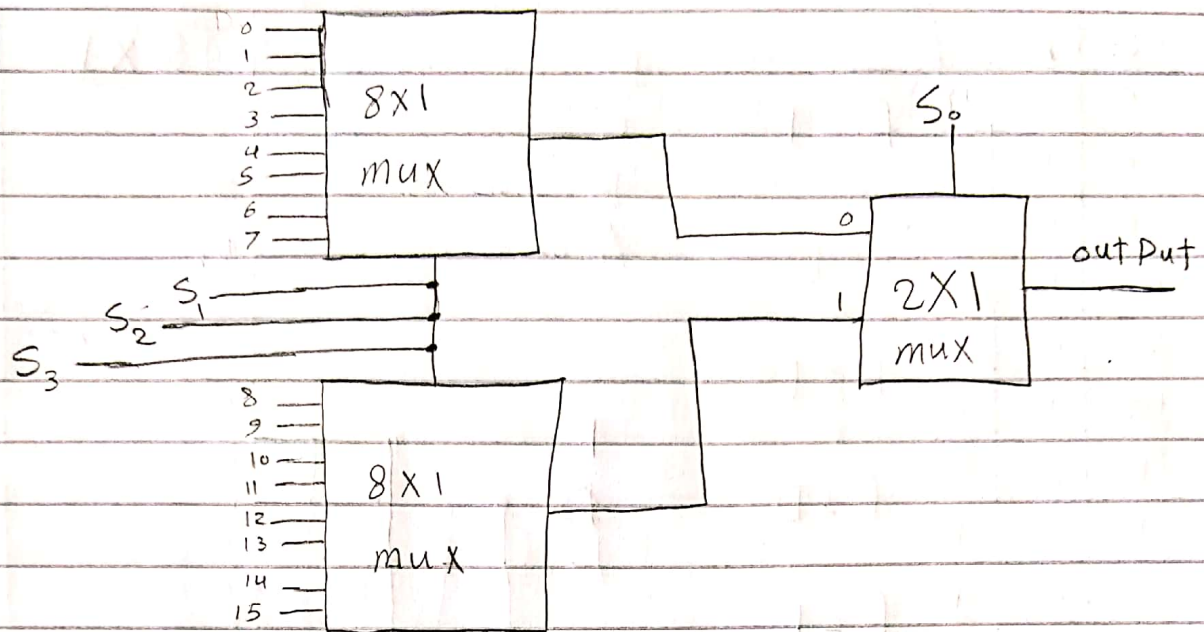
31. Construct a 16x1 multiplexer with two 8x1 and one 2x1 multiplexers. Using block diagrams.



32. Implement the following Boolean function with a multiplexer:


(a) $F(A, B, C, D) = \sum m(0, 2, 5, 8, 10, 14)$ $n-1 = 3$ $\text{mux} = 2^3 = 8 \times 1$
 Select lines

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

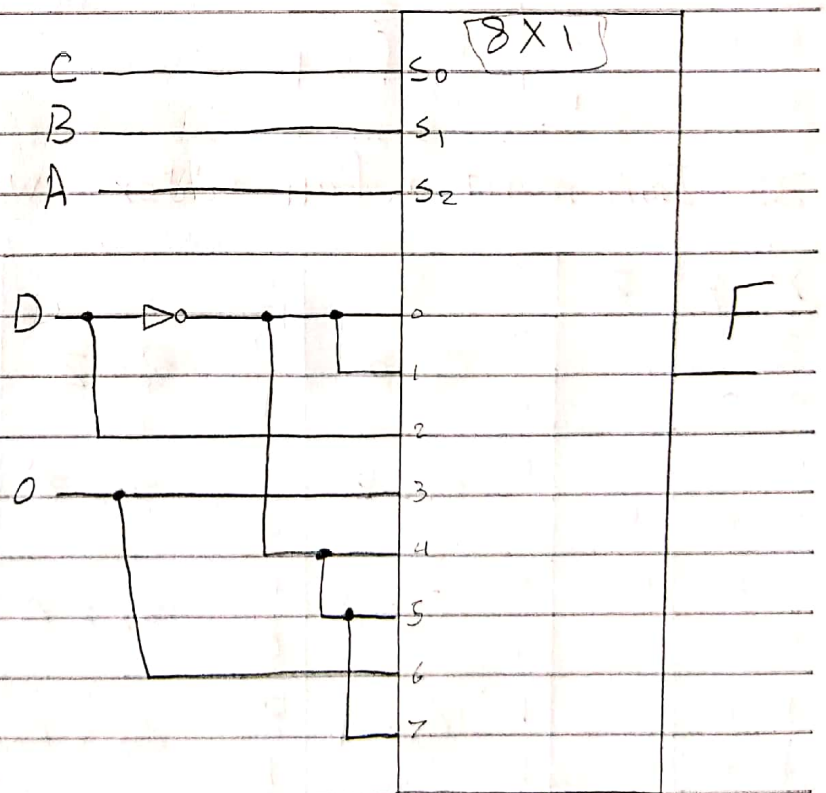

(b) $F(A, B, C, D) = \sum M(2, 6, 11)$

A	B	C	D	F				8x1
0	0	0	0	1	$F=1$	C	_____	S_0
0	0	0	1	1		B	_____	S_1
0	0	1	0	0	$F=D$	A	_____	S_2
0	0	1	1	1				
0	1	0	0	1	$F=1$			
0	1	0	1	1				
0	1	1	0	0	$F=D$			
0	1	1	1	1				
1	0	0	0	1	$F=1$			
1	0	0	1	1				
1	0	1	0	1	$F=D'$			
1	0	1	1	0				
1	1	0	0	1	$F=1$			
1	1	0	1	1				
1	1	1	0	1	$F=1$			
1	1	1	1	1				

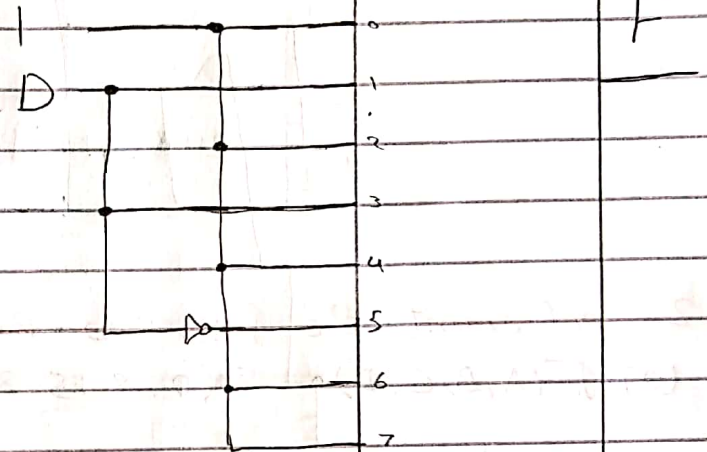

33- Implement a Full adder with two 2x1 multiplexer:-

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$C_0 = 0$

$S_0 = Z$

$C_1 = Z$

$S_1 = Z'$


$C_2 = Z$

$S_2 = Z'$

$C_3 = 1$

$S_3 = Z$

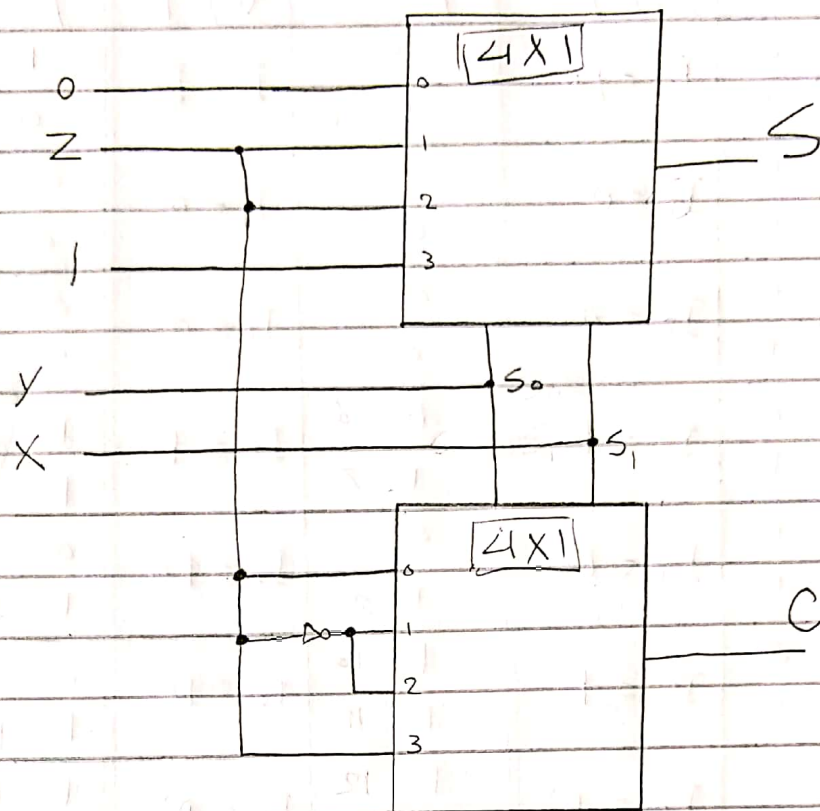→ Implementation of a full adder using two 4x1 multiplexer:-




34: An 8x1 multiplexer has inputs A, B, and C connected to selection inputs S_2, S_1, S_0 . The data inputs are as follows:-

(a) $I_1 = I_2 = I_3 = 0$

$I_3 = I_5 = 1$

$I_0 = I_4 = D$

$I_6 = D'$

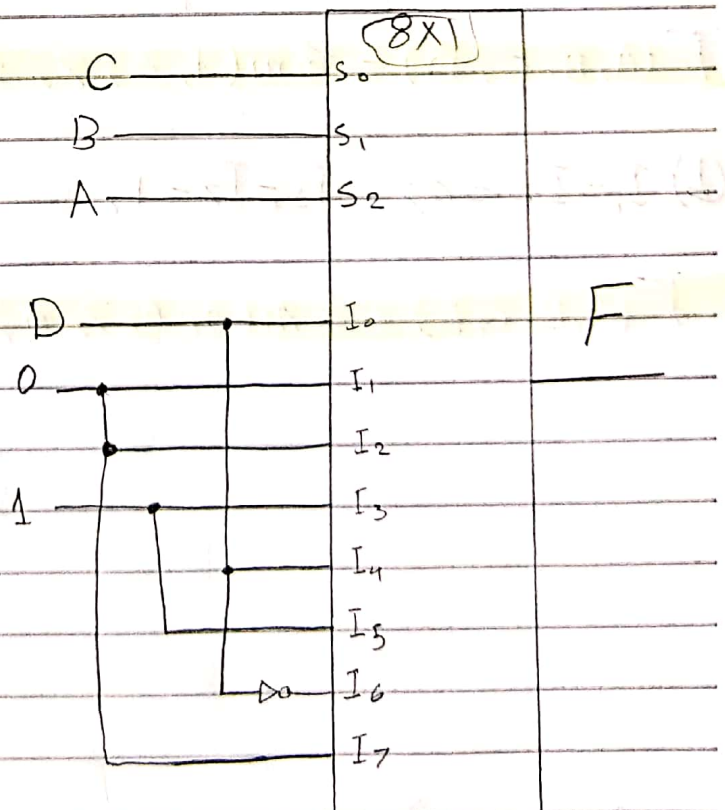

$$(a) I_1 = I_2 = I_7 = 0; \quad I_3 = I_5 = 1; \quad I_0 = I_4 = D; \quad I_6 = D'$$

A	B	C	D	(a) F	F =	(b) F	F =
0	0	0	0	$I_0 = D$	0	$I_0 = D'$	1 0
0	0	0	1		1 1		0
0	0	1	0	$I_1 = 0$	0	$I_1 = 0$	0
0	0	1	1		0		0
0	1	0	0	$I_2 = 0$	0	$I_2 = 0$	0
0	1	0	1		0		0
0	1	1	0	$I_3 = 1$	1 6	$I_3 = 1$	1 6
0	1	1	1		1 7		1 7
1	0	0	0	$I_4 = D$	0	$I_4 = D$	0
1	0	0	1		1 9		1 9
1	0	1	0	$I_5 = 1$	1 10	$I_5 = D$	0
1	0	1	1		1 11		1 11
1	1	0	0	$I_6 = D'$	1 12	$I_6 = D'$	1 12
1	1	0	1		0		0
1	1	1	0	$I_7 = 0$	0	$I_7 = 1$	1 14
1	1	1	1		0		1 15

$$F(A, B, C, D) = \sum m(1, 6, 7, 9, 10, 11, 12)$$

$$(b) I_1 = I_2 = 0; \quad I_3 = I_7 = 1; \quad I_4 = I_5 = D; \quad I_0 = I_6 = D'$$

$$F(A, B, C, D) = \sum m(0, 6, 7, 9, 11, 12, 14, 15)$$