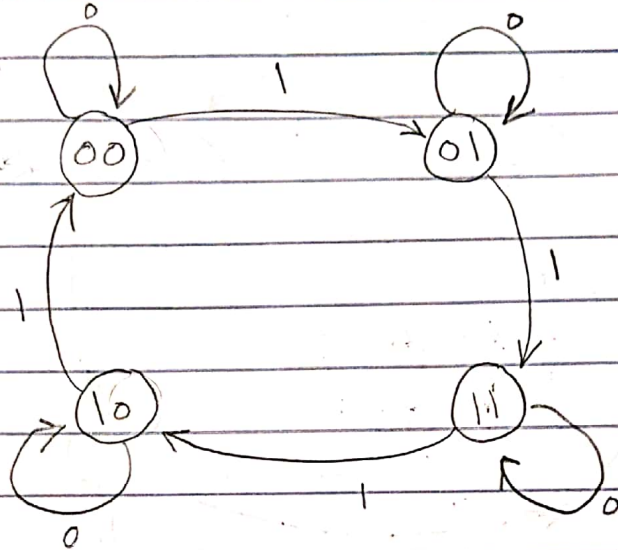


Exercise Seven

5.16 Design a sequential circuit with two D-FF A and B, and one input X.

(a) When $x_{in} = 0$, the state of the circuit remains the same. When $x_{in} = 1$, the circuit goes through the state transitions from $00 \rightarrow 01 \rightarrow 11 \rightarrow 10$ back to 00 , and repeats.

1- State diagram



2- State and assignment table

P.S	N.S		P.S	input		N.S	D _A	D _B
	X=0	X=1		A	B			
00	00	01	0	0	0	0	0	0
01	00	11	0	0	1	0	1	1
10	00	00	0	1	0	0	0	0
11	00	10	0	1	1	1	1	1
			1	0	0	0	0	0
			1	0	1	0	0	0
			1	1	0	0	0	0
			1	1	1	1	1	0

3- D-FF

Excitation table

Q	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

4- Simplified input equations


A \ Bx	00	01	11	10
0	0	1	1	1
1	1	1	1	1

A \ Bx	00	01	11	10
0	0	1	1	1
1	1	1	1	1

$$D_A = Bx$$


$$D_B = A'x$$

5-The Design

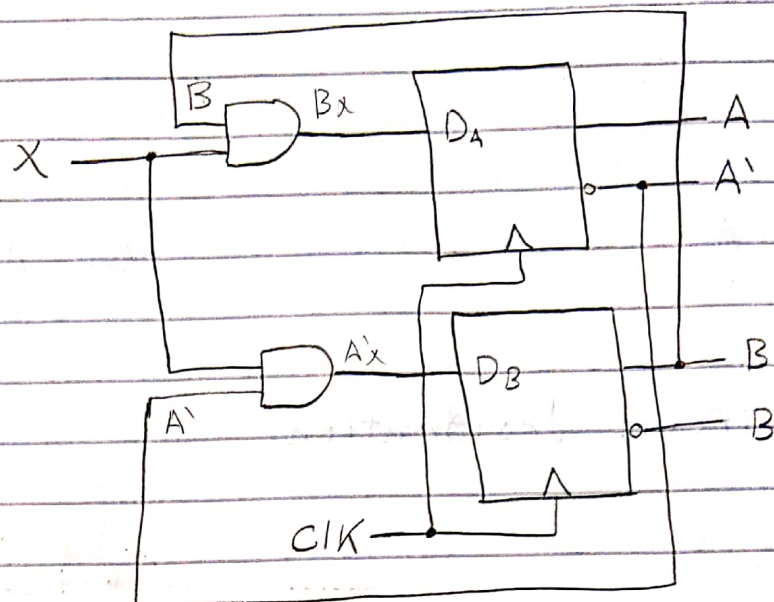

(B) When $x_{in}=0$, the state remains the same and
When $x_{in}=1$, the circuit goes through the state
transitions from $00 \rightarrow 01 \rightarrow 01 \rightarrow 10$, back to 00 ...

1- State diagram

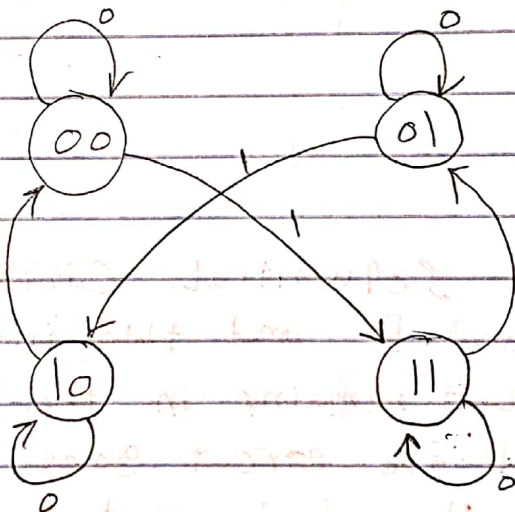

2- State table

P.S	N.S		P.S		input X	N.S		DA	DB
	X=0	X=1	A	B		A	B		
00	00	11	0	0	0	0	0	0	0
01	00	10	0	1	0	0	0	0	0
10	00	00	0	1	1	1	0	1	0
11	00	01	1	0	0	0	0	0	0
			1	0	1	0	0	0	0
			1	1	0	0	0	0	0
			1	1	1	0	1	0	1

3- Simplified input equations

$$D_A = \sum m(1, 3)$$

A \ Bx	00	01	11	10
0	0	1	1	2
1	4	5	7	6


$$D_A = A'x$$

$$D_B = \sum m(1, 7)$$

A \ Bx	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$\begin{aligned} D_B &= A'B'x + ABx \\ &= x(A'B' + AB) \\ &= x(A \oplus B)' \end{aligned}$$


4- Circuit designation.

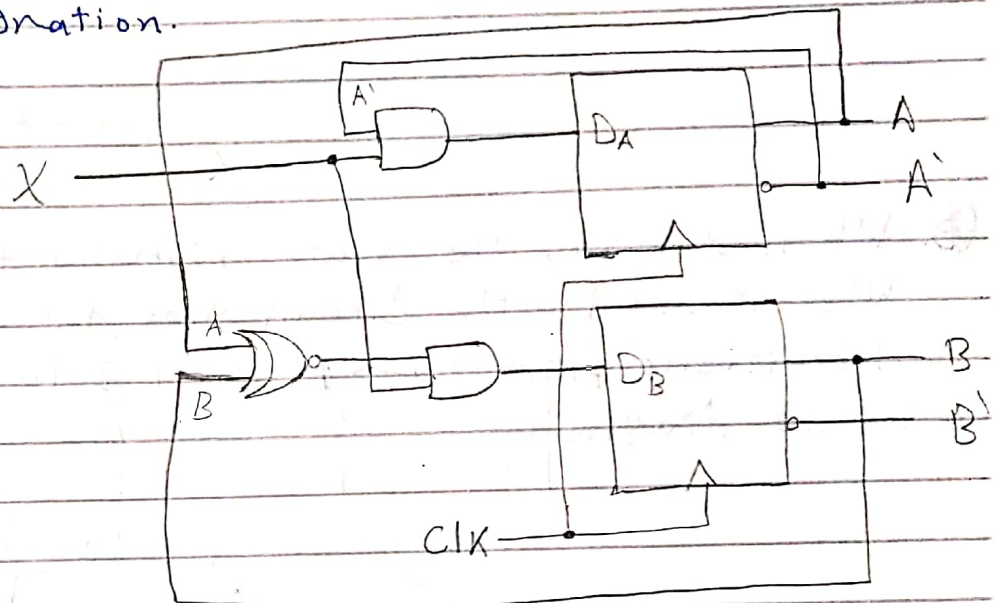

5.18 Design a sequential circuit with two JK flip-flops A and B and two inputs E and F. If $E=0$ the circuit remains in the same state, when $E=1$ & $F=1$ the circuit goes through from $00 \rightarrow 01 \rightarrow 10 \rightarrow 11$, and back to 00 .

When $E=1$ and $F=0$ it goes through $00 \rightarrow 11 \rightarrow 10 \rightarrow 01$ back to 00 .

1- State diagram

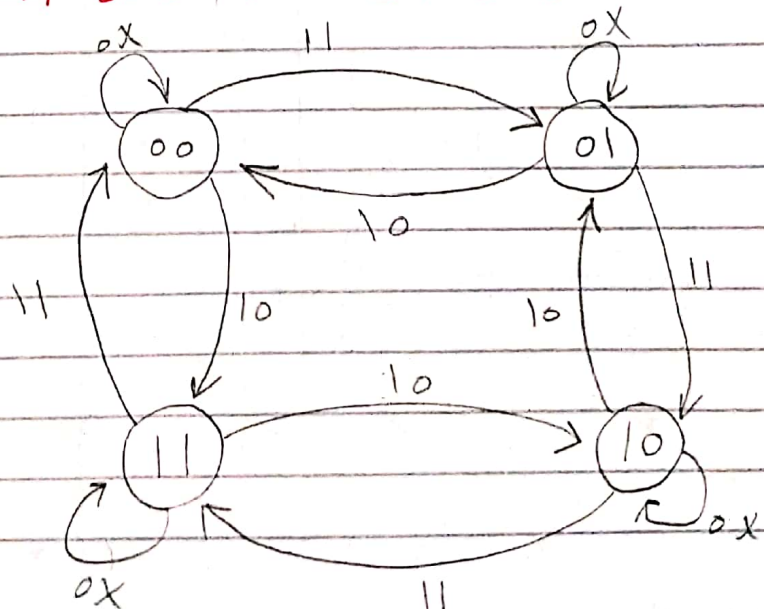

2- State table,

P.S		input		N.S		JA		KA		JB		KB	
A	B	E	F	A	B	JA	KA	JB	KB	JA	KB	JB	KB
0	0	0	X	0	0	0	X	0	X	0	X	0	X
0	0	0	X	0	0	0	X	0	X	0	X	0	X
0	0	1	0	1	1	1	X	1	X	1	X	1	X
0	0	1	1	0	1	0	X	1	X	1	X	1	X
0	1	0	X	0	1	0	X	X	0	X	0	X	0
0	1	0	X	0	1	0	X	X	0	X	0	X	0
0	1	1	0	0	0	0	X	X	1	X	1	X	1
0	1	1	1	1	0	1	X	X	1	X	1	X	1
1	0	0	X	1	0	X	0	0	X	0	X	0	X
1	0	0	X	1	0	X	0	0	X	0	X	0	X
1	0	1	0	0	1	X	1	1	X	1	X	1	X
1	0	1	1	1	1	X	1	1	X	1	X	1	X
1	1	0	X	1	1	X	0	X	0	X	0	X	0
1	1	0	X	1	1	X	0	X	0	X	0	X	0
1	1	1	0	1	0	X	0	X	1	X	1	X	1
1	1	1	1	0	0	X	1	X	1	X	1	X	1

3- JK-FF Transition Table

Q	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

4- Simplified functions

$$J_A = \sum m(2, 7) + d \sum (8, 9, 10, 11, 12, 13, 14, 15)$$

$$K_A = \sum m(10, 15) + d \sum m(0, 1, 2, 3, 4, 5, 6, 7)$$

AB \ EF	00	01	11	10
00	0	1	3	4 (1)
01	4	5	7 (1)	6
11	12 X	13 X	15 (X)	14 X
10	8 X	9 X	11 X	10 (X)

AB \ EF	00	01	11	10
00	0 X	1 X	3 X	4 (X)
01	4 X	5 X	7 (X)	6 X
11	12	13	15 (1)	14
10	8	9	11	10 (1)

$$\begin{aligned}
 J_A &= BEF + B'EF' \\
 &= E(BF + B'F') \\
 &= E(B \oplus F)'
 \end{aligned}$$

$$\begin{aligned}
 K_A &= BEF + B'EF' \\
 &= E(BF + B'F') \\
 &= E(B \oplus F)'
 \end{aligned}$$

$$J_B = \sum m(2, 3, 10, 11) + d \sum m(4, 5, 6, 7, 12, 13, 14, 15)$$


AB \ EF	00	01	11	10
0			1	1
4	X	X	X	X
12	X	X	X	X
8			1	1

$$J_B = E$$

$$K_B = \sum m(6, 7, 14, 15) + d \sum m(0, 1, 2, 3, 8, 9, 10, 11)$$

AB \ EF	00	01	11	10
0	X	X	X	X
4		5	7	6
12		13	15	14
8	X	9	11	10

$$K_B = E$$

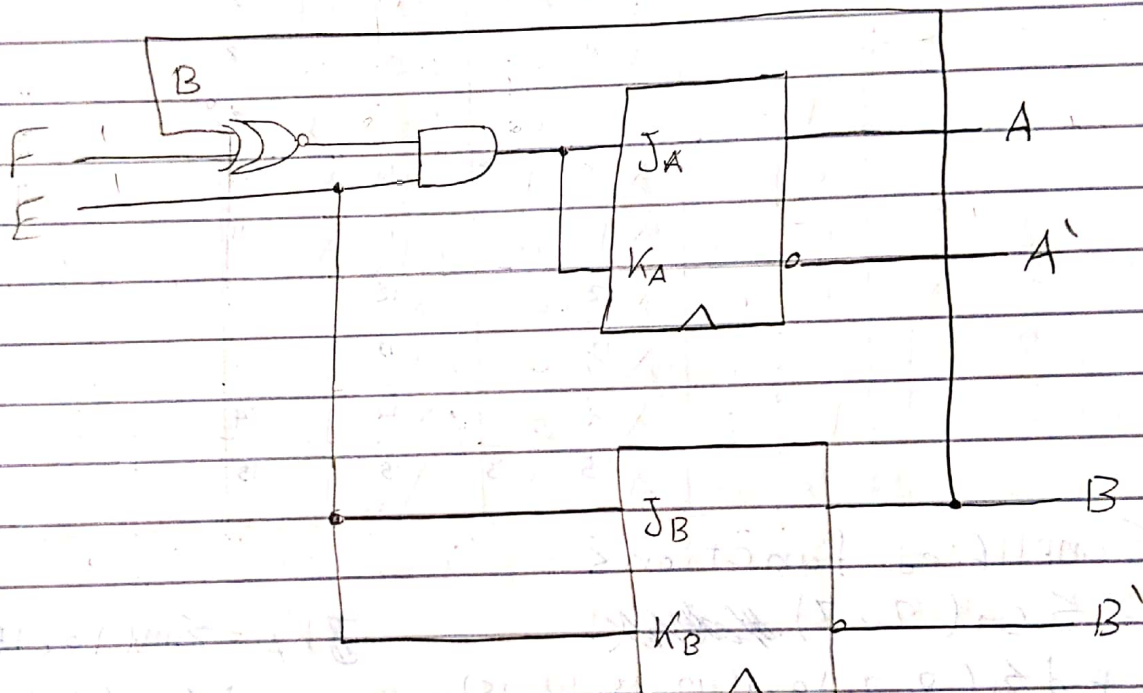

5.19 A Sequential Circuit has three flip-flops A, B, C; one input x-in; and one output y-out. The State diagram is shown in Fig. P.5.19. Analyze the circuit obtained from the design to determine the effect of the unused state.

(a) Use D-FFs in the design.

1) State table:-

P.S	Next State		output		JK excitation table			
	x=0	x=1	x=0	x=1				
000	011	100	0	1	Q	Q _(t+1)	J	K
001	001	100	0	1				
010	010	000	0	1				
011	001	010	0	1				
100	010	011	0	0				
					1	1	X	0

P.S	x-in	N.S	y-out	J _A	K _A	J _B	K _B	J _C	K _C	D _A	D _B	D _C
000	0	011	0	0	X ⁰	1 ⁰	X ⁰	1 ⁰	X ⁰	0	1 ⁰	1 ⁰
000	1	100	1	1 ¹	X ¹	0	X ¹	0	X ¹	1 ¹	0	0
001	0	001	0	0	X ²	0	X ²	X ²	0	0	0	1 ²
001	1	100	1	1 ³	X ³	0	X ³	X ³	1 ³	1 ³	0	0
010	0	010	0	0	X ⁴	X ⁴	0	0	X ⁴	0	1 ⁴	0
010	1	000	1	0	X ⁵	X ⁵	1 ⁵	0	X ⁵	0	0	0
011	0	001	0	0	X ⁶	X ⁶	1 ⁶	X ⁶	0	0	0	1 ⁶
011	1	010	1	0	X ⁷	X ⁷	0	X ⁷	1 ⁷	0	1 ⁷	0
100	0	010	0	X ⁸	1 ⁸	1 ⁸	X ⁸	0	X ⁸	0	1 ⁸	0
100	1	011	0	X ⁹	1 ⁹	1 ⁹	X ⁹	1 ⁹	X ⁹	0	1 ⁹	1 ⁹

Simplified Functions:-

don't care = $\sum m(10, 11, 12, 13, 14, 15)$

$D_A = \sum m(1, 3)$

$D_B = \sum m(0, 4, 7, 8, 9)$

$D_C = \sum m(0, 2, 6, 9)$

AB \ Cx	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	X	13	X
10	8	9	11	X

$$D_A = A'B'x$$

AB \ Cx	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	X	13	X
10	8	9	11	X

$$D_B = Cx' + A + BCx$$


AB \ Cx	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	X	13	X
10	8	9	11	X

$$D_C = A'B'x' + Ax + Cx'$$

Designation ^{with} ~~off~~ x D-FFs

$$D_A = A'B'x$$
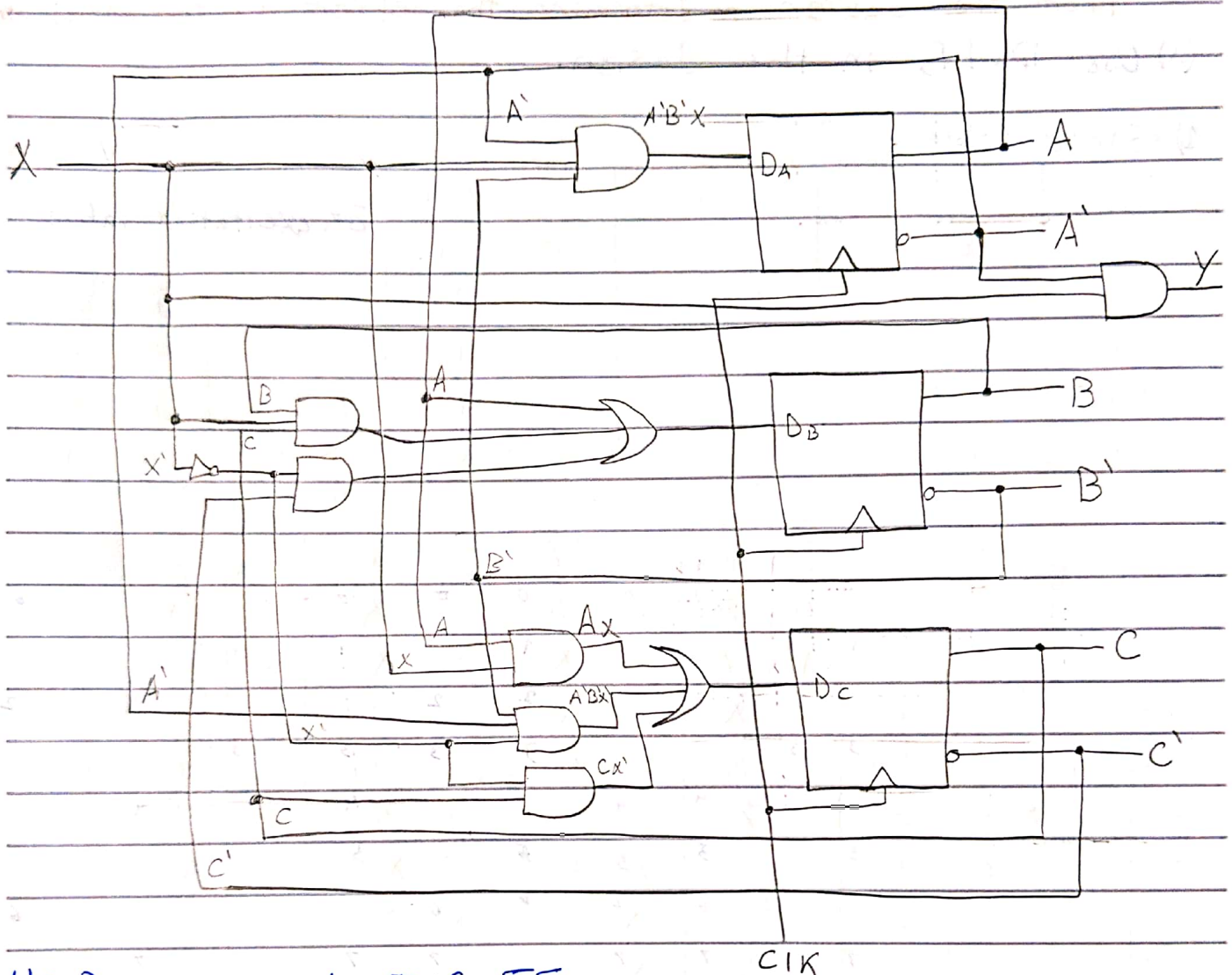
$$D_B = A + Bcx + C'x' \quad D_C = Ax + A'B'x' + Cx'$$



(b) Design with JK-FFs

$$J_A = \sum m(1, 3)$$

$$K_A = \sum m(8, 9)$$

$$+d = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

$$+d = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 10, 11, 12, 13, 14, 15)$$

AB \ Cx	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

AB \ Cx	0	1	3	2
4	X	X	X	X
12	X	X	X	X
8	1	1	X	X

$$K_A = 1$$

$$J_A = B'x$$

$$J_B = \sum m(10, 8, 9) + d \sum m(4, 5, 6, 7, 10, 11, 12, 13, 14, 15)$$

AB \ Cx	00	01	11	10
00	0 1	1	3	2
01	4 X	5 X	7 X	6 X
11	12 X	13 X	15 X	14 X
10	8 1	9 1	11 X	10 X

$$J_B = C'x' + A$$

$$K_B = \sum m(5, 6) + d = \sum m(0, 1, 2, 3, 8, 9, 10, 11, \dots)$$

AB \ Cx	00	01	11	10
00	0 X	1 X	3 X	2 X
01	4	5 1	7	6 1
11	12 X	13 X	15 X	14 X
10	8 X	9 X	11 X	10 X

$$K_B = C'x + Cx' = C \oplus x$$

$$J_C = \sum m(0, 9) + d = \sum m(2, 3, 6, 7, 10, 11, \dots)$$

AB \ Cx	00	01	11	10
00	0 1	1	3 X	2 X
01	4	5	7 X	6 X
11	12 X	13 X	15 X	14 X
10	8	9 1	11 X	10 X

$$J_C = A'B'x' + Ax$$

$$K_C = \sum m(1, 7) + d = \sum m(0, 1, 4, 5, 8, 9, \dots)$$

AB \ Cx	00	01	11	10
00	0 X	1 1	3	2
01	4 X	5 X	7 1	6
11	12 X	13 X	15 X	14 X
10	8 X	9 X	11 X	10 X

$$K_C = C' + Bx$$

$$\text{out} = y = \sum m(1, 3, 5, 7) + d = \sum m(10, 11, 12, 13, 14, 15)$$

AB \ Cx	00	01	11	10
00	0	1 1	3 1	2
01	4	5 1	7 1	6
11	12 X	13 X	15 X	14 X
10	8	9	11 X	10 X

$$y = A'x$$

$$J_A = B'x$$

$$K_A = 1$$


$$y =$$

$$J_B = A + Cx'$$

$$K_B = C \oplus x$$

$$J_C = A'B'x' + Ax$$

$$K_C = Bx + C'$$

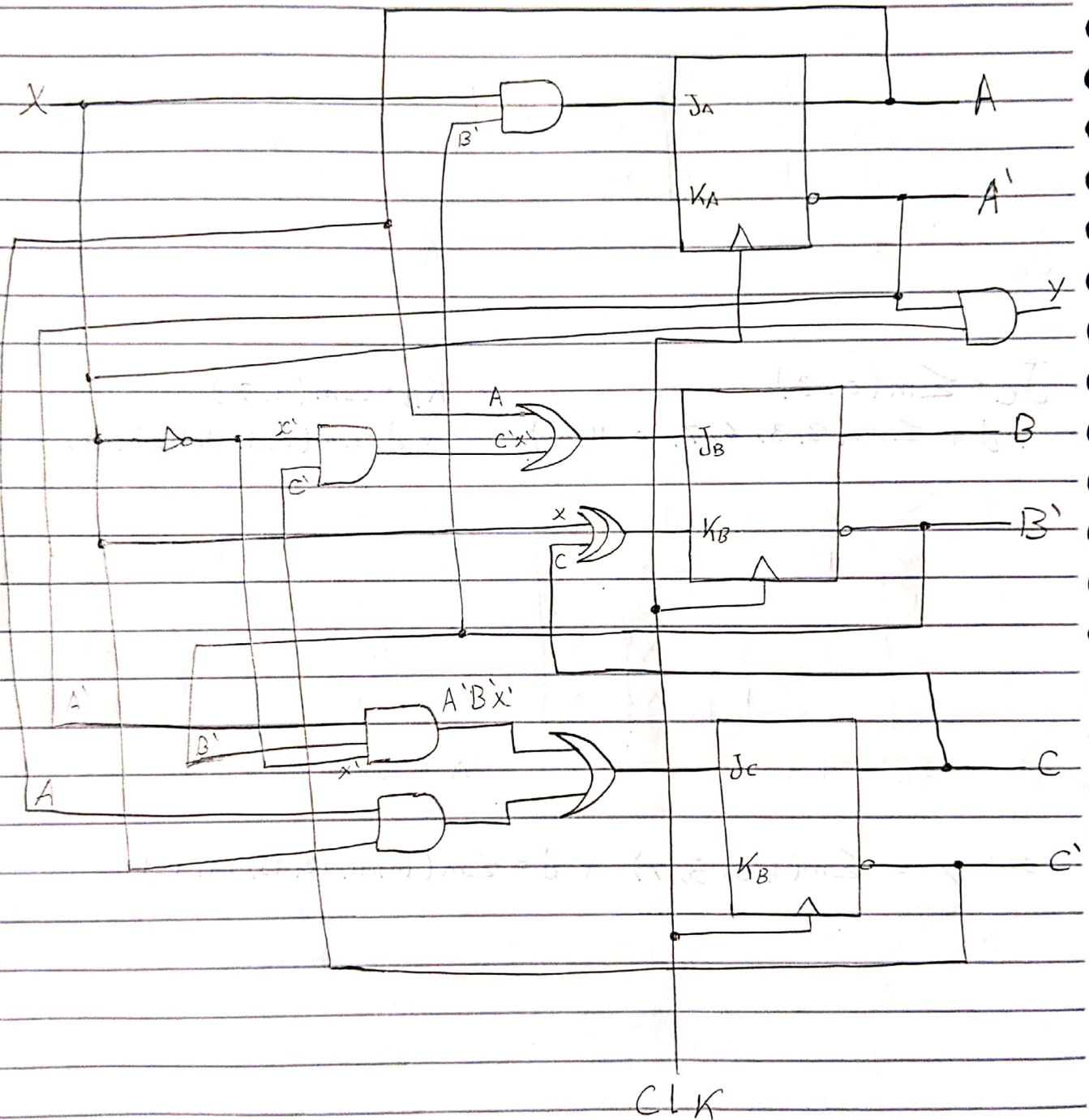

5.20 Design the sequential circuit specified by the state diagram of Fig. 5.19, using T-FFs

1- State table

P.S	Next State		Present-State		Input x	Next-State		T _A	T _B
	x=0	x=1	A	B		A	B		
S ₀	S ₁	S ₀	0	0	0	0	1	0	1 ⁰
S ₁	S ₃	S ₂	0	0	1	0	0	0	0
S ₂	S ₃	S ₃	0	1	0	1	1	1 ²	0
S ₃	S ₀	S ₃	0	1	1	1	0	1 ³	1 ³
			1	0	0	1	1	0	1 ⁴
			1	0	1	1	1	0	1 ⁵
			1	1	0	0	0	1 ⁶	0
			1	1	1	1	1	0	1 ⁷

T-FF Excitation table

Q	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

$$T_A = \sum m(2, 3, 6)$$

$$T_B = \sum m(0, 3, 4, 5, 7)$$

A \ Bx	00	01	11	10
0	0	1	3	2
1	4	5	7	6

A \ Bx	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$T_A = A'B + Bx'$$

$$\begin{aligned} T_B &= B'x' + AB' + Ax + Bx \\ &= AB' + Bx + B'x' \\ &= AB' + (B \oplus x)' \end{aligned}$$

